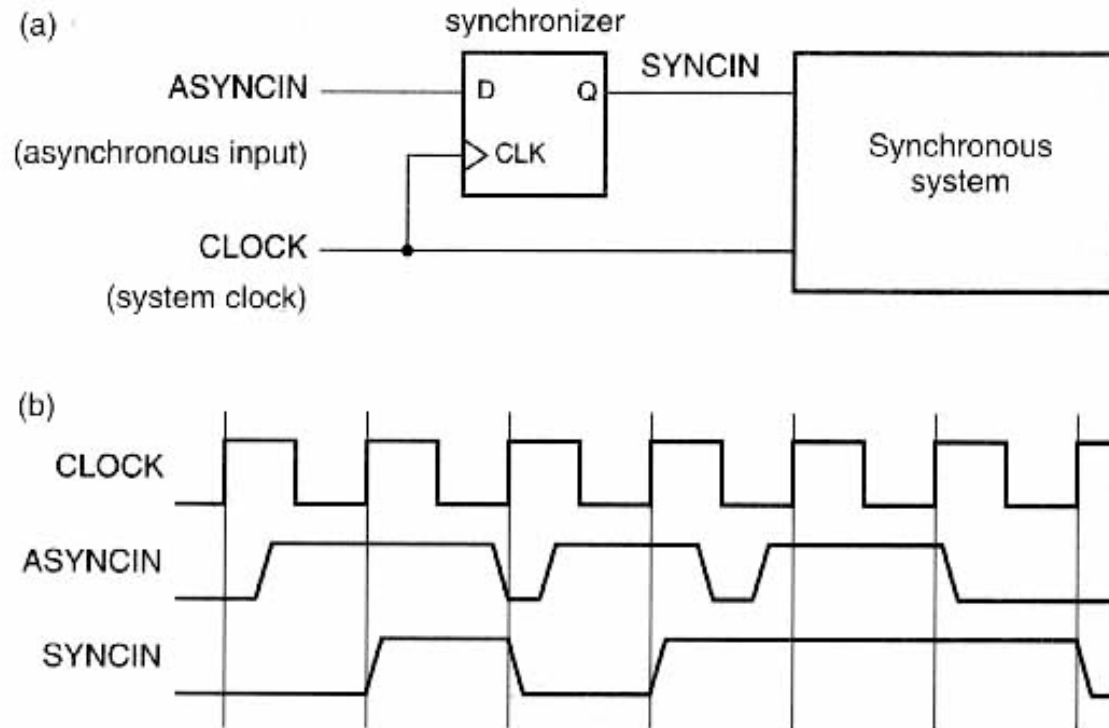


Asynchronous Inputs to Synchronous Systems

- Many synchronous systems need to interface to asynchronous input signals:
 - Consider a computer system running at some clock frequency, say 1GHz with:
 - Interrupts from I/O devices, keystrokes, etc.
 - Data transfers from devices with their own clocks
 - Ethernet has its own 100MHz clock
 - PCI bus transfers, 66MHz standard clock.
 - These signals could have no known timing relationship with the system clock of the CPU.
 - (On FPGAs we can use FIFOs - separate clocks for input and output - as the interface. In general, this is overkill - and too expensive).

“Synchronizer” Circuit


- For a single asynchronous input, we use a simple flip-flop to bring the external input signal into the timing domain of the system clock:



- The D flip-flop samples the asynchronous input at each cycle and produces a synchronous output that meets the setup time of the next stage.

“Synchronizer” Circuit

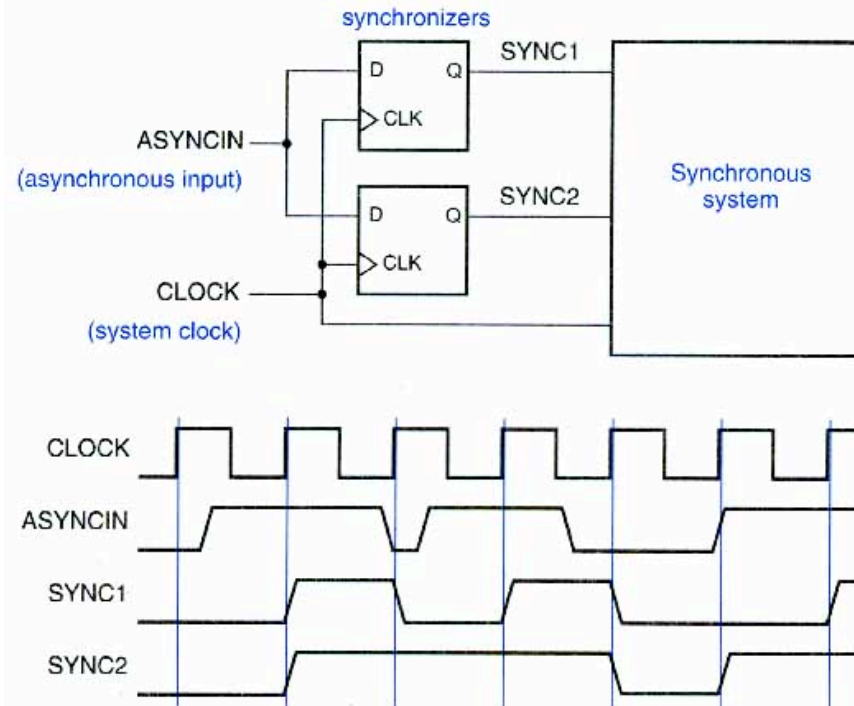
- It is essential for asynchronous inputs to be synchronized at only one place.



- Two flip-flops may not receive the clock and input signals at precisely the same time (*clock and data skew*).
- When the asynchronous changes near the clock edge, one flip-flop may sample input as 1 and the other as 0.

“Synchronizer” Circuit



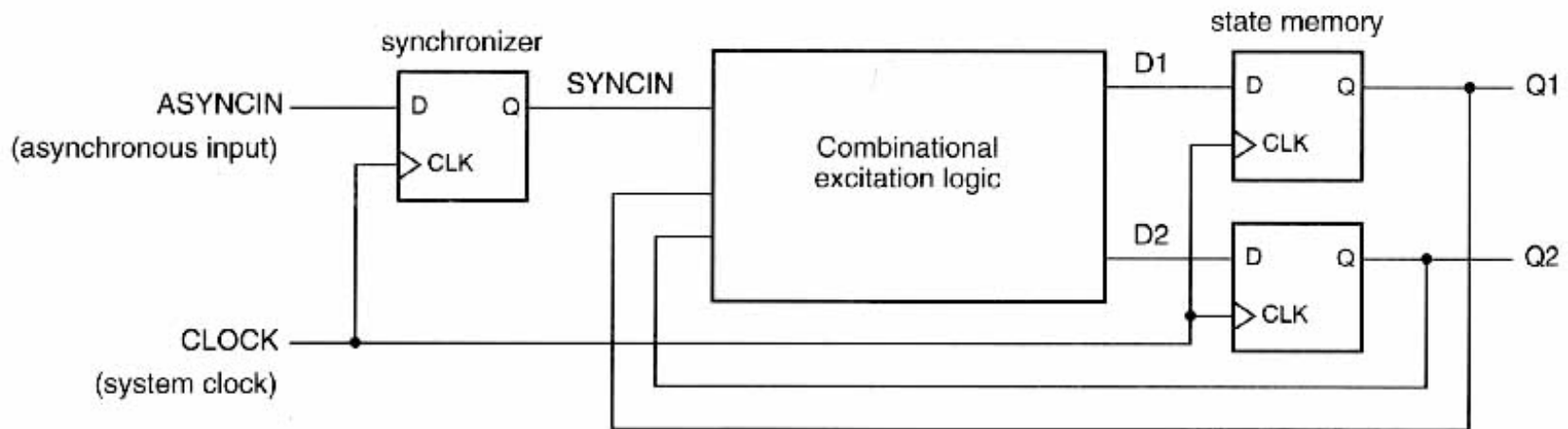
- Single point of synchronization is even more important when input goes to a combinational logic block (ex. FSM)
- The CL block can accidentally hide the fact that the signal is synchronized at multiple points.
- The CL magnifies the chance of the multiple points of synchronization seeing different values.



- Sounds simple, right?

Synchronizer Failure & Metastability

- We think of flip-flops having only two stable states - but all have a third *metastable* state halfway between 0 and 1.
- When the setup and hold times of a flip-flop are not met, the flip-flop could be put into the metastable state.
- Noise will be amplified and push the flip-flop one way or other.
- However, in theory, the time to transition to a legal state is unbounded.
- Does this really happen?
- The probability is low, but number of trials is high!

   

Transfer function:

$$V_{out1} = T(V_{in1})$$


$$V_{out2} = T(V_{in2})$$

Synchronizer Failure & Metastability

- If the system uses a synchronizer output while the output is still in the metastable state \Rightarrow synchronizer failure.
- Initial versions of several commercial ICs have suffered from metastability problems - effectively synchronization failure:
 - AMD9513 system timing controller
 - AMD9519 interrupt controller
 - Zilog Z-80 Serial I/O interface
 - Intel 8048 microprocessor
 - AMD 29000 microprocessor
- To avoid synchronizer failure wait long enough before using a synchronizer's output. *“Long enough”, according to Wakerly, is so that the mean time between synchronizer failures is several orders of magnitude longer than the designer's expected length of employment!*
- In practice all we can do is reduce the probability of failure to a vanishing small value.

Reliable Synchronizer Design

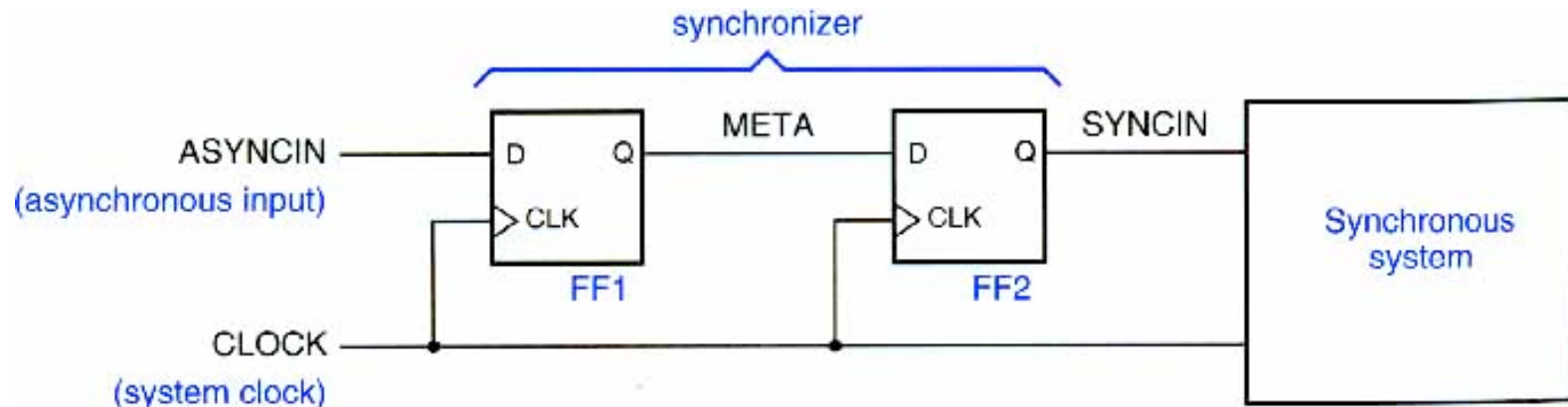- The probability that a flip-flop stays in the metastable state decreases exponentially with time.
- Therefore, any scheme that delays using the signal can be used to decrease the probability of failure.
- In practice, delaying the signal by a cycle is usually sufficient:



- If the clock period is greater than metastability resolution time plus **FF2** setup time, **FF2** gets a synchronized version of **ASYN CIN**.
- Multi-cycle synchronizers (using counters or more cascaded flip-flops) are even better - but often overkill.